

Timing analysis / pipelining

V1.0

- ▶ Overview of timing report generated by Vivado
- ▶ How pipelining can improve you timings
- ▶ Workshop

Franck Jullien



@fjullien06



<https://github.com/fjullien>



Report file - check_timing_report

- ▶ *_timing.rpt
- ▶ check_timing report → error report

Table of Contents

-
- 1. checking no clock (0)
- 2. checking constant clock (0)
- 3. checking pulse width clock (0)
- 4. checking unconstrained internal endpoints (0)
- 5. checking no input delay (8)
- 6. checking no output delay (4)
- 7. checking multiple clock (0)
- 8. checking generated clocks (0)
- 9. checking loops (0)
- 10. checking partial input delay (0)
- 11. checking partial output delay (0)
- 12. checking latch loops (0)

Can be ignored most
of the time

Report file - Design Timing Summary

- ▶ WNS → Worst Negative Setup slack
- ▶ WHS → Worst Hold Slack
- ▶ WNS and WHS must be greater than or equal to zero

WNS(ns)

-0.755

TNS(ns)

-4.588

TNS Failing Endpoints

10

TNS Total Endpoints

146

WHS(ns)

0.263

THS(ns)

0.000

...

...

...

Most influenced by
your design

Report file - Max Delay Paths

Max Delay Paths

```
-----  
Slack (VIOLATED) :      -0.755ns  (required time - arrival time)  
Source:                xilinxmultiregimpl0 regs1 reg/C  
                        (rising edge-triggered cell FDRE clocked by clk100  
Destination:           b reg[29]/D  
                        (rising edge-triggered cell FDRE clocked by clk100  
Path Group:            clk100  
Path Type:             Setup (Max at Slow Process Corner)  
Requirement:           10.000ns  (clk100 rise@10.000ns - clk100 rise@0.000ns)  
Data Path Delay:        10.790ns  (logic 7.724ns (71.586%) route 3.066ns (28.414%))  
Logic Levels:          7  (CARRY4=3 DSP48E1=2 LUT3=1 LUT6=1)  
Clock Path Skew:       -0.039ns  (DCD - SCD + CPR)  
  Destination Clock Delay (DCD):    4.795ns = ( 14.795 - 10.000 )  
  Source Clock Delay (SCD):         5.093ns  
  Clock Pessimism Removal (CPR):    0.259ns  
Clock Uncertainty:      0.035ns  ((TSJ^2 + TIJ^2)^1/2 + DJ) / 2 + PE  
  Total System Jitter (TSJ):        0.071ns  
  Total Input Jitter (TIJ):         0.000ns  
  Discrete Jitter (DJ):             0.000ns  
  Phase Error (PE):                 0.000ns
```


Visual inspection

2 – Select the entire netlist

1 - Open the timing report


3 - Open the schematic

4 – Select the failing path

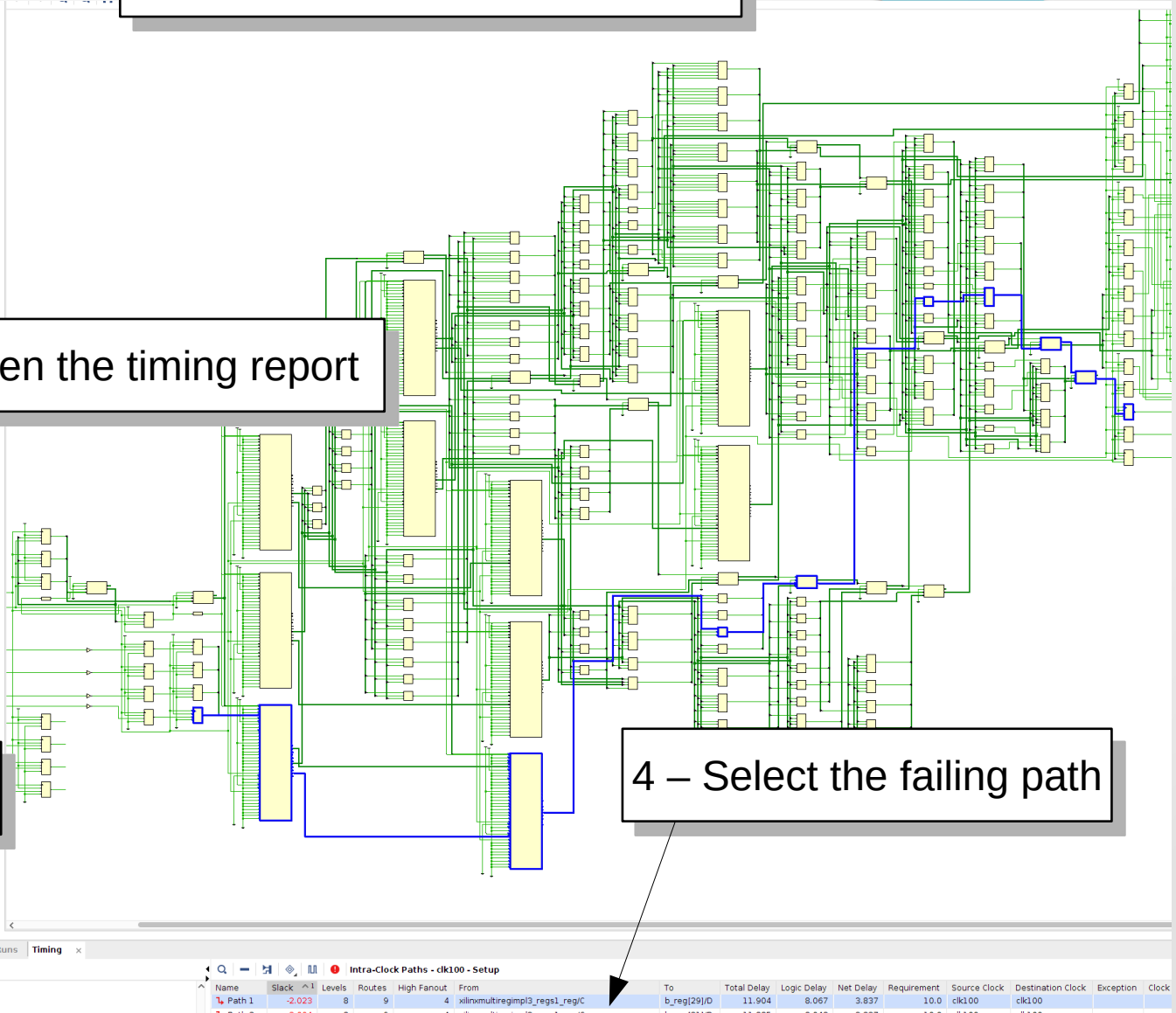


Visual inspection

Open the elaborated schematic

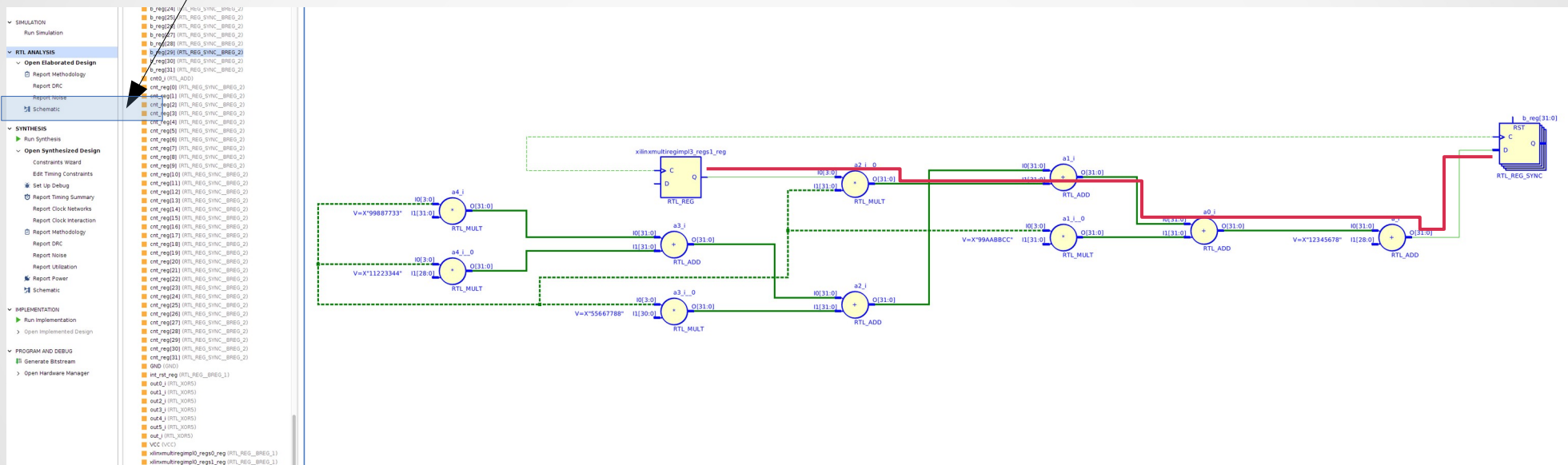


Pipelining

 - ▶ Long combinatorial path can be *cut* into smallest chunks
- ▶ We insert registers to *cut* combinatorial path
- ▶ Latency is introduced



Pipelining

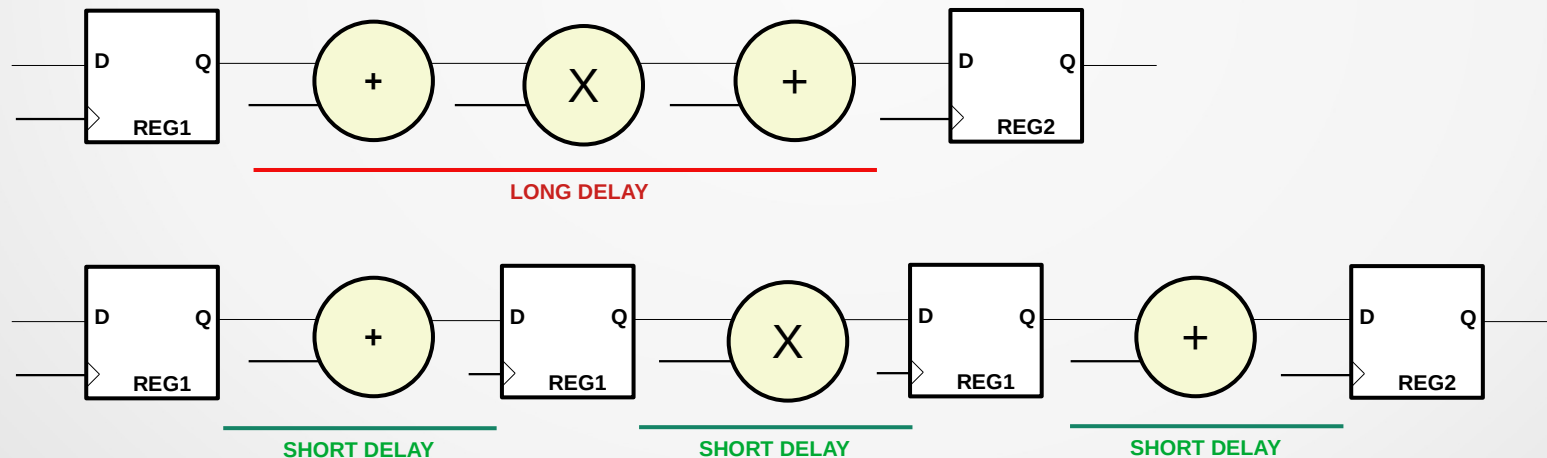- ▶ Long combinatorial path can be *cut* into smallest chunks
- ▶ We insert registers to *cut* combinatorial path
- ▶ Latency is introduced



Workshop - extra0

- ▶ Build the non pipelined version of workshop_extra0
- ▶ Look at the timing report, open Vivado and look at the RTL schematics
- ▶ Design the pipelined version of workshop_extra0
- ▶ Make sure it works :)
- ▶ Look at the timing report, open Vivado and look at the RTL schematics